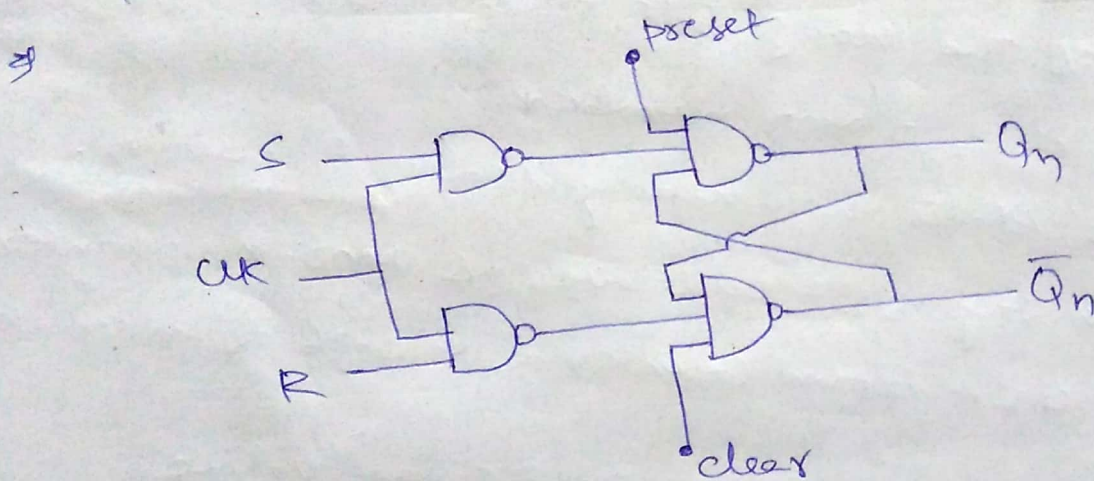


Preset and clear inputs

- these are called direct inputs or overriding inputs or asynchronous inputs.
- These are called overriding inputs because independent of flipflop inputs when these inputs are present, o/p of the flip flop changes.



Here, when $\text{preset} = 0 \Rightarrow Q_n = 1$

when $\text{clear} = 0 \Rightarrow \bar{Q}_n = 1 \Rightarrow Q_n = 0$

whatever be the clock and inputs of the flipflop, ~~then~~
when $\text{preset} = 0$ my Q_n value is 1. Similarly,
when $\text{clear} = 0$ my Q_n value is 0.

→ If preset and clear are equal to 1, then flipflop performs normally and it is independent of preset and clear inputs.

(Note: Roll Numbers should not be written)

Modules of the Counter & Counting to particular value

- ⇒ 2 bit ripple counter is called MOD-4 or modulus 4 counter.
- ⇒ 3 bit ripple counter is called MOD-8 or modulus 8 counter.
- ⇒ If n is the no. of bits then MOD number = 2^n .
no. of states = MOD number.
- ⇒ Modulus states how many states it having.
- ⇒ So we can say 3 bit up counter as MOD-8 up counter.
Similarly, 4 bit down counter as MOD-16 down counter.

⇒ How to stop counting upto particular value

Ex Design MOD-6 counter using MOD-8 counter.

Now we have to design MOD-8 counter.

MOD-8 means 3 bit counter. we can design either up/down counter. from MOD-8 counter we have to design MOD-6 counter. i.e. it must have 6 states and max. count is 5.

In MOD-8 counter,

$$\text{no. of states} = 8$$

$$\text{no. of bits} = 3$$

$$\text{no. of FF's} = 3$$

$$\text{max count} = 8 - 1 = 7$$

where as in MOD-6 counter,


$$\text{no. of states} = 6$$

$$\text{no. of bits} = 3$$

$$\text{no. of FF's} = 3$$


$$\text{max count} = 6 - 1 = 5$$

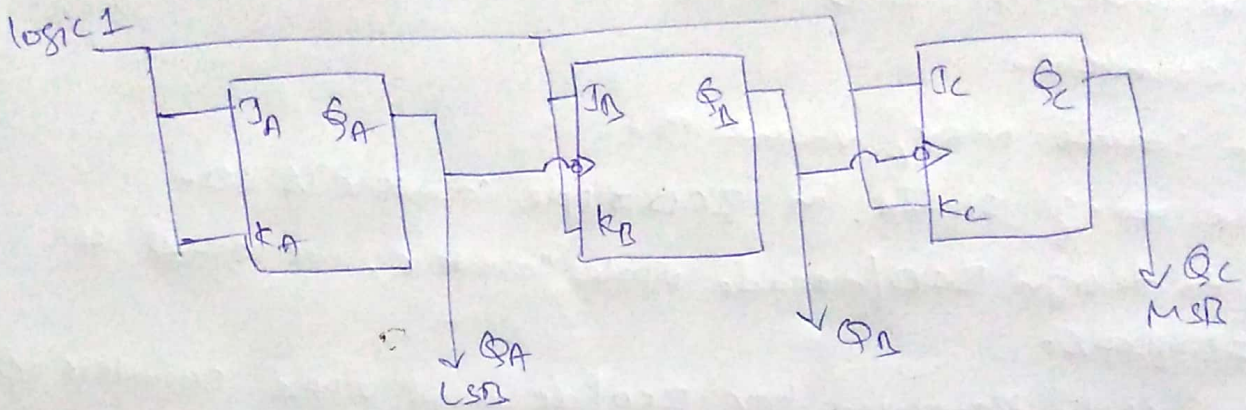First we have to design MOD-8 counter. Here i'm considering up counter.



From this Mod-8 counter, we have to design Mod-6 Counter. For this, i use preset and clear inputs. I give preset input to logic 1. So the circuit is independent of preset input. But Mod-8 Counter counts upto 7. But here in Mod-6 Counter, max, count is 5 only. So when it counts Mod-8 Counter counts is 5 only. So when it counts 5, then it acts as 5, after that next count is 0, then it acts as Mod-6 Counter. for that, we give clear i/p = 0 when Mod8 Counter counts 6.

$6 = 110$

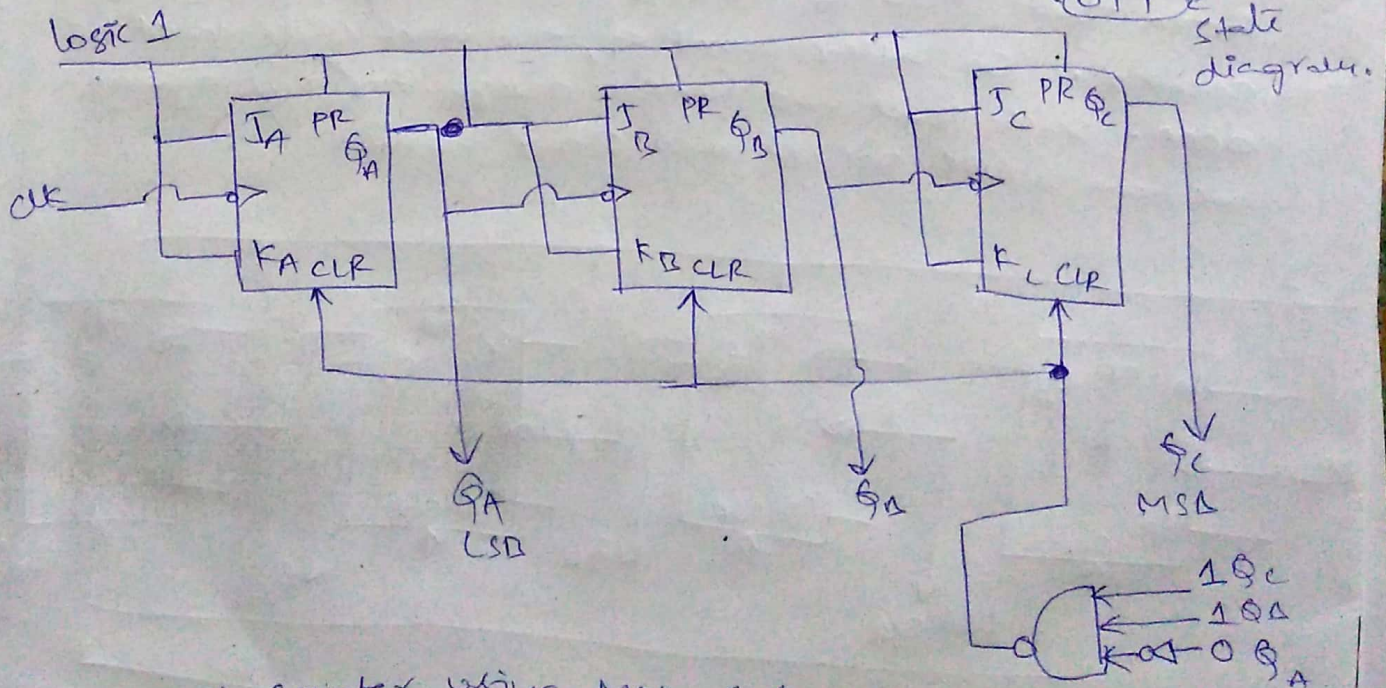

MOD-6 counter using MOD-8 Counter.

Decode (BCD) ripple counter


⇒ Decode (or) BCD ripple counter means Mod-10 counter.

it counts max. value 9.

the no. of states in BCD ripple counter is 10.


So to design BCD/decode ripple counter, we need 4 flipflops.

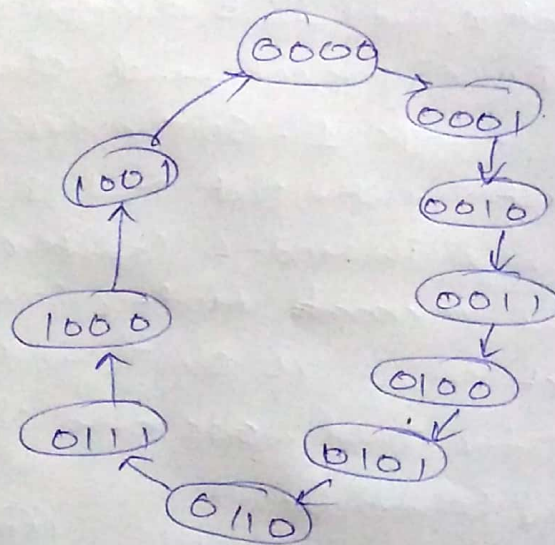the state diagram for BCD/decimal ripple counter is,



Now we have to design $2^4 = 16$ i.e. MOD 16 counter.

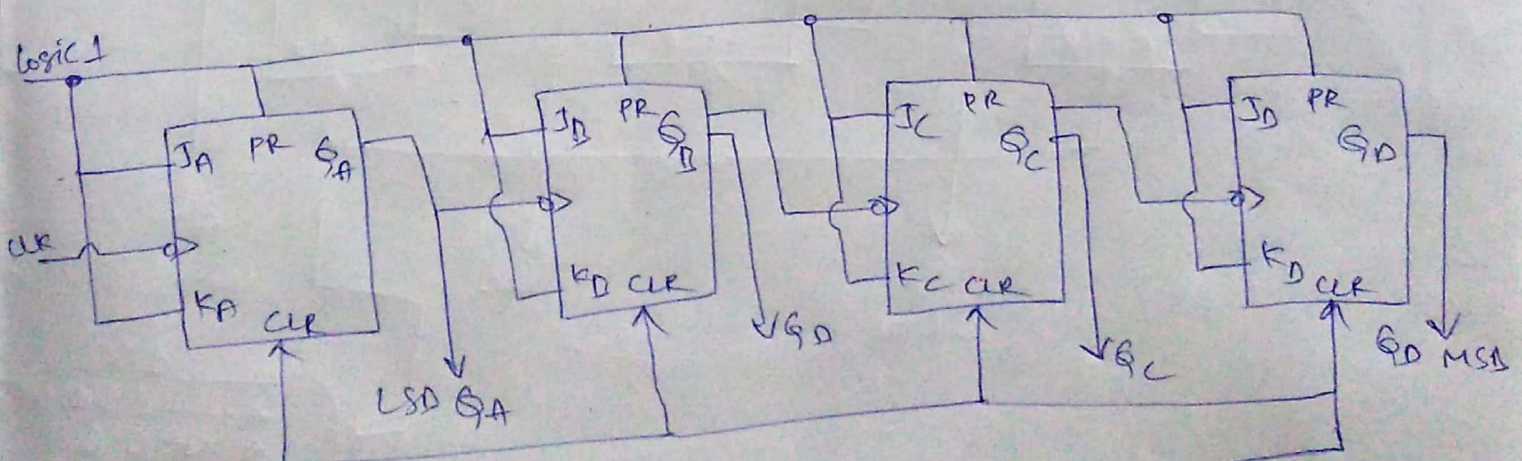From that MOD-16 counter, we develop MOD 10/BCD counter. So, after count 9, the next state must be 0000. Such that we have to design for this again we have to use preset and clear inputs.



MOD-10 counter using MOD-16 counter.

